

Lec 8: Equivalent circuit & Efficiency of Transformer


Outline:

1) Electric Equivalent circuit of single Phase transformer
الدائرة الكهربائية المكافئة للحوّل آتاري الوحد

2) Calculation of losses & Efficiency
حساب الخسائر و الكفاءة

Transformer → Principle of operation & Construction
→ e.m.f equation & turns ratio (نسب التحويل)
→ No load & loading cases
→ Equivalent circuit & Efficiency

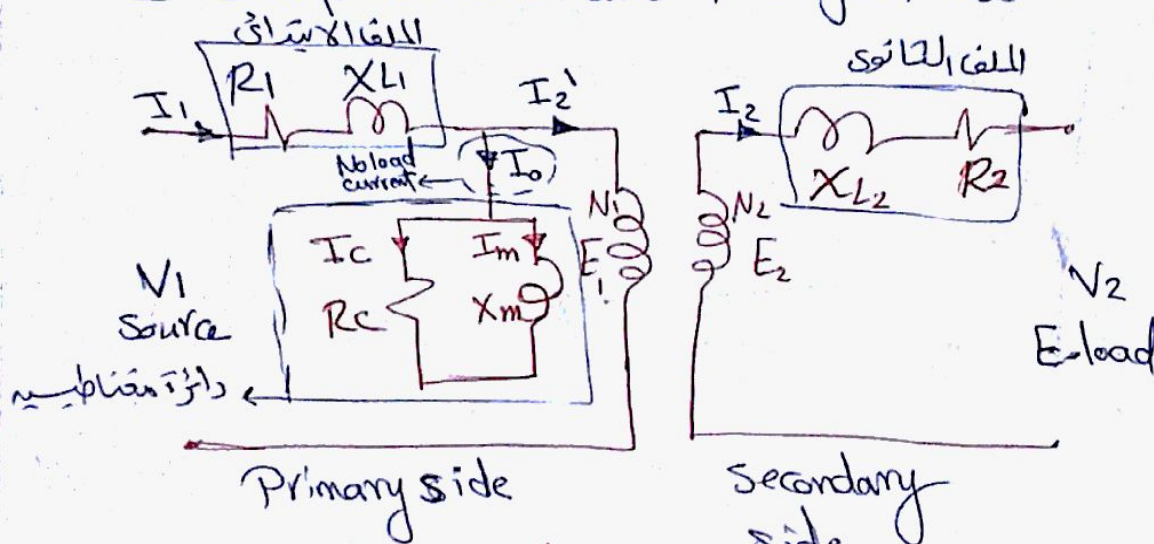3) E. Equivalent circuit of single Phase transformer.



* Equivalent circuit of 1- ϕ transformer.

R_1 & R_2 : Primary and secondary resistance (Ω)

X_1 & X_2 : Primary and secondary inductance reactance (Ω)

N_1 & N_2 : No of turns of Primary & Secondary

I_0 : No load current (A)

I_c : Core losses current (A)

I_m : magnetizing current (A)


V_1 : Voltage of source (V)

V_2 : terminal voltage (V)


E_1 & E_2 : induced emf in Primary & Secondary

R_c : resistance of magnetizing circuit

X_m : reactance of magnetizing circuit.

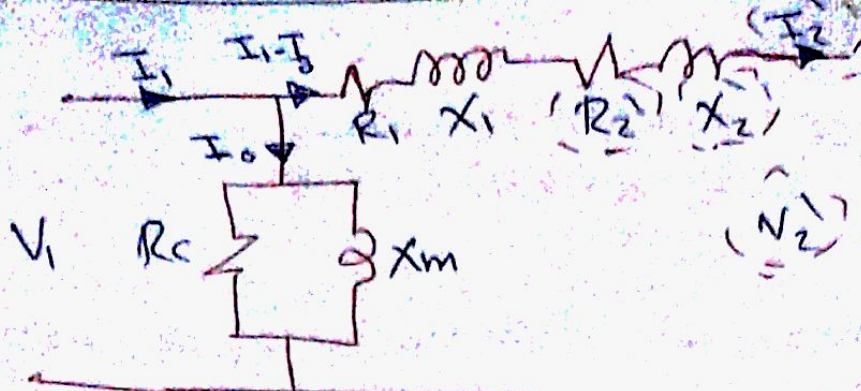

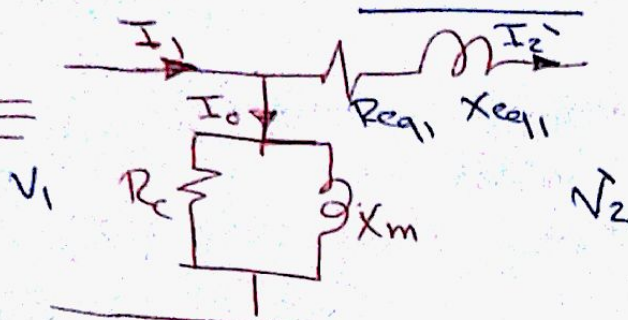Equivalent circuit referred to Primary side
الدائرة المكافئة المنسوبة إلى الملف الابتدائي



$$X_{eq1} = X_1 + X_2'$$

$$R_{eq1} = R_1 + R_2'$$

$$Z = \sqrt{R_{eq1}^2 + X_{eq1}^2}$$

$$I_2^2 R_2 = I_1^2 R_2'$$

$$R_2' = R_2 \left(\frac{I_2}{I_1} \right)^2 = R_2 \left(\frac{V_1}{V_2} \right)^2$$

$$R_2' = R_2 \left(\frac{N_1}{N_2} \right)^2, \quad X_2' = X_2 \left(\frac{N_1}{N_2} \right)^2$$

$$\therefore X_{eq} = X_1 + X_2' = X_1 + X_2 \left(\frac{N_1}{N_2} \right)^2$$

$$R_{eq} = R_1 + R_2' = R_1 + R_2 \left(\frac{N_1}{N_2} \right)^2$$

Example: A transformer has 600 Primary turns & 150 Secondary turns. the Primary & Secondary resistance are 0.125 Ω, 0.01 Ω respectively. the corresponding leakage reactance are 0.15 Ω, 0.04 Ω respectively.

Find @ Equivalent circuit referred to Primary winding
① " " " " secondary winding

Given:

$$N_1 = 600, N_2 = 150, R_1 = 0.125 \Omega, R_2 = 0.01 \Omega$$

$$X_1 = 0.15 \Omega, X_2 = 0.04 \Omega$$

@ $R_{eq1} = R_1 + R_2', \quad X_{eq} = X_1 + X_2'$

② $R_{eq2} = R_1' + R_2, \quad X_{eq} = X_1' + X_2$

I_1 (input current) \rightarrow I_2 (loading current) \rightarrow I_0 \rightarrow I_m flux (ϕ) \rightarrow I_c \rightarrow (losses)


*** سؤال مهم

Explain the losses of [Dc machine, transformer,]

شرح الخسائر في (المحرك، المحوّل،)

** Losses in transformer

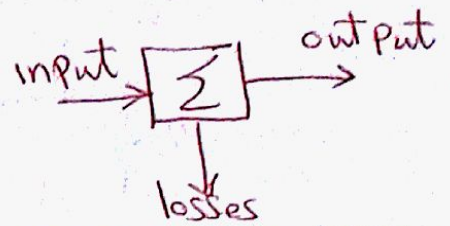- \rightarrow Copper (Electrical) losses
- \rightarrow Iron (Magnetizing) losses
- \rightarrow No Mechanical losses



$$\text{input} = \text{output} + \text{losses}$$

قد تصل كفاءة المحوّل إلى 98,99%

Efficiency of transformer η % "eta"

$$\eta \% = \frac{X S \cos \theta}{X S \cos \theta + P_{\text{core}} + X^2 P_{\text{Cu}}} \times 100\%$$

S = rating of transformer [KVA] = $I \times V_{\text{rated}}$

X = fraction of loading

$\cos \theta$ = Power factor of load

P_{Cu} = Copper losses = $I_1^2 R_1 + I_2^2 R_2$

P_{core} = Core losses

Max efficiency occur at $x = ?$

$$\eta_{\max} \% = \frac{SGS\theta}{SGS\theta + \frac{P_{core}}{x} + xP_{cu}}$$



$\frac{d}{dx}$ (denominator) = Zero

$$\frac{d}{dx} \left(SGS\theta + \frac{P_{core}}{x} + xP_{cu} \right)$$

$$x^2 P_{cu} = P_{core}$$

دراخت بوس
سبب سبب
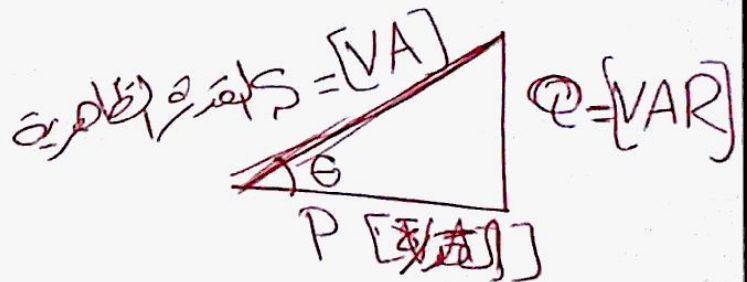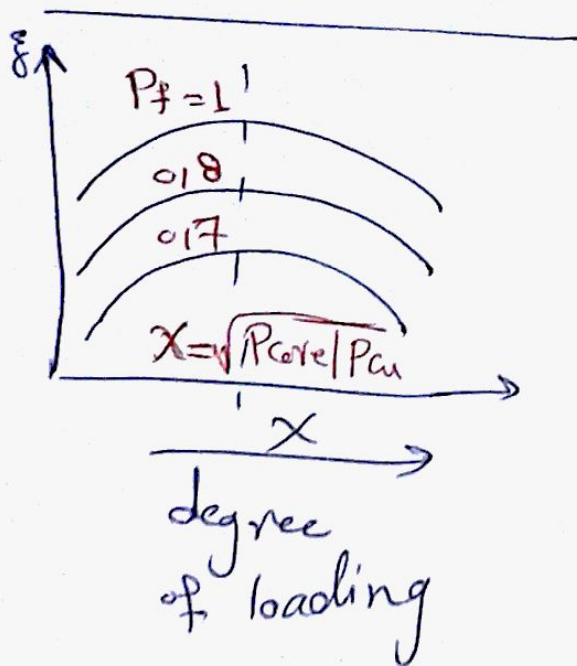
$$\therefore x = \sqrt{\frac{P_{core}}{P_{cu}}}$$



Max efficiency occur at $x = ?$
 (X) $x = \sqrt{\frac{P_{core}}{P_{cu}}} = 1$
 Max efficiency occur at $x = 1$
 (X) $x = \sqrt{\frac{P_{core}}{P_{cu}}} = 1$
 Max efficiency occur at $x = 1$
 (X) $x = \sqrt{\frac{P_{core}}{P_{cu}}} = 1$